 


Problem 1:

Truth table:

G	T	U	E	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Devre Şeması:




Kodlar:


```
C:/Users/Esra/Documents/quartusmodelsim/lab1_g8_p1.sv (/tb_lab1_g8_p1/dut0) - Default
Ln#
1 // Y = G?IU?E + GIUE + GI?U?E + GIU?E + G?IUE + G?I?UE + GIUE?
2 module lab1_g8_p1(
3     input logic g, t, u, e,
4     output logic y
5 );
6
7 assign y = ~g & t & ~u & e | g & t & u & e | g & ~t & ~u & e | g & t & ~u & e | ~g & t & u & e | ~g & ~t & u & e | g & t & u & ~e;
8
9 endmodule
10
```

```
Ln#
1 module tb_lab1_g8_p1 ();
2     logic g_tb, t_tb, u_tb, e_tb;
3     logic y_tb;
4
5
6     lab1_g8_p1 dut0(g_tb, t_tb, u_tb, e_tb, y_tb);
7
8     initial begin
9
10         g_tb = 0; t_tb = 0; u_tb = 0; e_tb = 0; #10
11         e_tb = 1; #10
12         u_tb = 1; e_tb = 0; #10
13         e_tb = 1; #10
14         t_tb = 1; u_tb = 0; e_tb = 0; #10
15         e_tb = 1; #10
16         u_tb = 1; e_tb = 0; #10
17         e_tb = 1; #10
18         g_tb = 1; t_tb = 0; u_tb = 0; e_tb = 0; #10
19         e_tb = 1; #10
20         u_tb = 1; e_tb = 0; #10
21         e_tb = 1; #10
22         t_tb = 1; u_tb = 0; e_tb = 0; #10
23         e_tb = 1; #10
24         u_tb = 1; e_tb = 0; #10
25         g_tb = 1; t_tb = 1; u_tb = 1; e_tb = 1; #10
26
27         $stop;
28     end
29
30
31 endmodule
32
```

Zaman Diyagramı:

 

Quartus:

Flow Summary	
 <<Filter>>	
Flow Status	Successful - Thu Apr 27 23:08:19 2023
Quartus Prime Version	22.1std.1 Build 917 02/14/2023 SC Lite Edition
Revision Name	lab1_g8_p1
Top-level Entity Name	lab1_g8_p1
Family	MAX 10
Device	10M08DAF484C8G
Timing Models	Final
Total logic elements	2 / 8,064 (< 1 %)
Total registers	0
Total pins	5 / 250 (2 %)
Total virtual pins	0
Total memory bits	0 / 387,072 (0 %)
Embedded Multiplier 9-bit elements	0 / 48 (0 %)
Total PLLs	0 / 2 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 1 (0 %)

Analysis & Synthesis Summary

 <<Filter>>


Analysis & Synthesis Status	Successful - Thu Apr 27 23:08:10 2023
Quartus Prime Version	22.1std.1 Build 917 02/14/2023 SC Lite Edition
Revision Name	lab1_g8_p1
Top-level Entity Name	lab1_g8_p1
Family	MAX 10
Total logic elements	1
Total registers	0
Total pins	5
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

Analysis & Synthesis Resource Usage Summary

 <<Filter>>

	Resource	Usage
1	Estimated Total logic elements	1
2		
3	Total combinational functions	1
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	1
2	-- 3 input functions	0
3	-- <=2 input functions	0
5		
6	▼ Logic elements by mode	
1	-- normal mode	1
2	-- arithmetic mode	0
7		
8	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
9		
10	I/O pins	5
11		
12	Embedded Multiplier 9-bit elements	0
13		
14	Maximum fan-out node	y~0
15	Maximum fan-out	1
16	Total fan-out	10
17	Average fan-out	0.91

Devre Şeması:

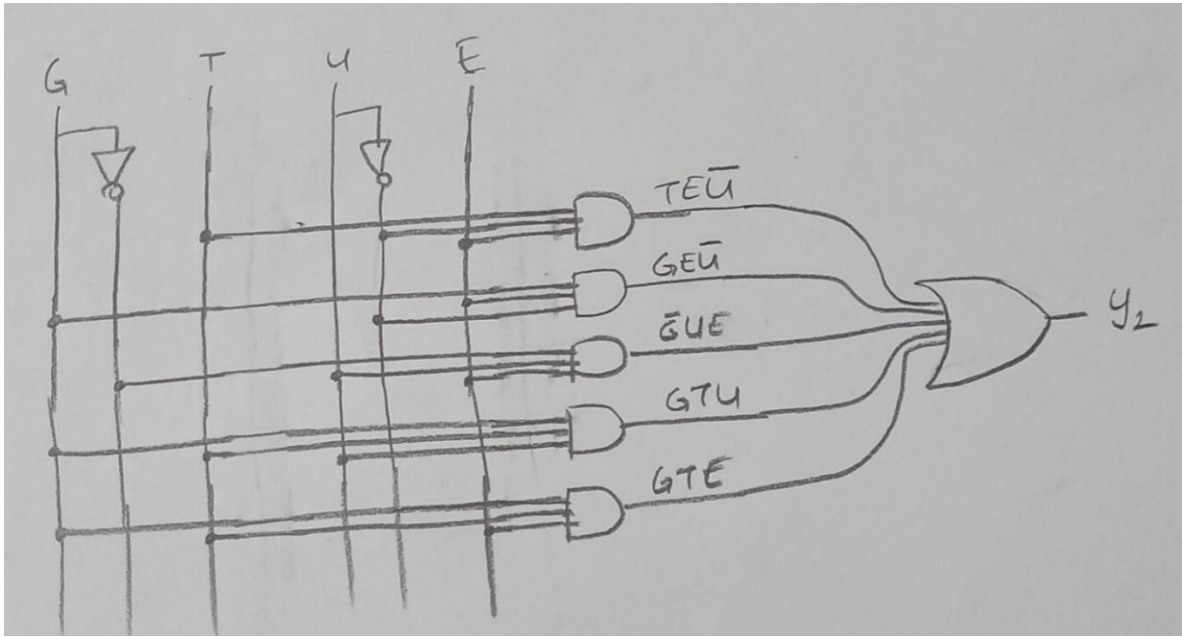

Kodlar:

```
D:/repos/Lojik/Lojik_Lab1/lab1_g8_p2.sv (/tb_lab1_g8_p2/dut0) - Default
Ln#
1
2 // Y = TEU'+GEU'+G'UE+GTU+GTE
3 module lab1_g8_p2(
4     input logic g, t, u, e,
5     output logic y
6 );
7
8 assign y = tse~u | gse~u | ~gsue | gtsu | gtsse;
9
10 endmodule
```


Quartus:

Flow Summary

 <<Filter>>

Flow Status	Successful - Fri Apr 28 00:03:40 2023
Quartus Prime Version	22.1std.1 Build 917 02/14/2023 SC Lite Edition
Revision Name	lab1_g8_p2
Top-level Entity Name	lab1_g8_p2
Family	MAX 10
Device	10M08DAF484C8G
Timing Models	Final
Total logic elements	2 / 8,064 (< 1 %)
Total registers	0
Total pins	5 / 250 (2 %)
Total virtual pins	0
Total memory bits	0 / 387,072 (0 %)
Embedded Multiplier 9-bit elements	0 / 48 (0 %)
Total PLLs	0 / 2 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 1 (0 %)

Analysis & Synthesis Summary

 <<Filter>>


Analysis & Synthesis Status	Successful - Fri Apr 28 00:03:32 2023
Quartus Prime Version	22.1std.1 Build 917 02/14/2023 SC Lite Edition
Revision Name	lab1_g8_p2
Top-level Entity Name	lab1_g8_p2
Family	MAX 10
Total logic elements	1
Total registers	0
Total pins	5
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

Analysis & Synthesis Resource Usage Summary

<<Filter>>

	Resource	Usage
1	Estimated Total logic elements	1
2		
3	Total combinational functions	1
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	1
2	-- 3 input functions	0
3	-- <=2 input functions	0
5		
6	▼ Logic elements by mode	
1	-- normal mode	1
2	-- arithmetic mode	0
7		
8	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
9		
10	I/O pins	5
11		
12	Embedded Multiplier 9-bit elements	0
13		
14	Maximum fan-out node	y~0
15	Maximum fan-out	1
16	Total fan-out	10
17	Average fan-out	0.91

lab1_g8_p2:1

 

Problem 3:

Truth table:

E	U	T	G	X	Y
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	1	0	1
1	0	1	0	0	1
1	0	1	1	0	1
1	1	0	0	0	1
1	1	0	1	0	0
1	1	1	0	0	1
1	1	1	1	0	0

X Sadeleştirme:

$$\begin{aligned}
 & \bar{E}\bar{U}\bar{T}\bar{G} + \bar{E}\bar{U}\bar{T}G + \bar{E}U\bar{T}\bar{G} + \bar{E}U\bar{T}G + \bar{E}U\bar{T}\bar{G} + \bar{E}UTG \\
 & \bar{E}\bar{U}\bar{T}(\bar{G} + G) + \bar{E}U\bar{T}(\bar{G} + G) + \bar{E}UT(\bar{G} + G) \\
 & \bar{E}\bar{U}\bar{T} + \bar{E}U(\bar{T} + T) \\
 & \bar{E}\bar{U}\bar{T} + \bar{E}U \rightarrow \bar{E}(\bar{U}\bar{T} + U) \\
 & \bar{E}((\bar{U} + U) \cdot (\bar{T} + T)) \\
 & \bar{E}(\bar{T} + \bar{U})
 \end{aligned}$$

Y sadeleştirme:

$$\begin{aligned} & E\bar{U}T\bar{G} + E\bar{U}\bar{T}G + \bar{E}U\bar{T}\bar{G} + \bar{E}\bar{U}TG \\ & E\bar{U}\bar{G}(\bar{T}+T) + \bar{E}\bar{U}\bar{G}(\bar{T}+T) \\ & \bar{U}\bar{G}(\bar{E}+E) = \bar{U}\bar{G} \end{aligned}$$


Kod ve Çıktılar:

```
D:/repos/Lojik/Lojik_Lab1/tb_lab1_g8_p3.sv (/tb_lab1_g8_p3) - Default
Ln#
2
3 module tb_lab1_g8_p3 ();
4     logic g_tb, t_tb, u_tb, e_tb;
5     logic x_tb;
6     logic y_tb;
7
8     lab1_g8_p3 dut0(g_tb, t_tb, u_tb, e_tb, x_tb, y_tb);
9     //lab1_g8_p3 dut0(g_tb, t_tb, u_tb, e_tb, y_tb);
10
11
12 initial begin
13
14     g_tb = 0; t_tb = 0; u_tb = 0; e_tb = 0; #10
15     g_tb = 1; #10
16     t_tb = 1; g_tb = 0; #10
17     g_tb = 1; #10
18     u_tb = 1; t_tb = 0; g_tb = 0; #10
19     g_tb = 1; #10
20     t_tb = 1; g_tb = 0; #10
21     g_tb = 1; #10
22     e_tb = 1; t_tb = 0; u_tb = 0; g_tb = 0; #10
23     g_tb = 1; #10
24     t_tb = 1; g_tb = 0; #10
25     g_tb = 1; #10
26     t_tb = 0; u_tb = 1; g_tb = 0; #10
27     g_tb = 1; #10
28     t_tb = 1; g_tb = 0; #10
29     g_tb = 1; t_tb = 1; u_tb = 1; g_tb = 1; #10
30
31     $stop;
32 end
33
```


```

D:/repos/Lojik/Lojik_Lab1/lab1_g8_p3.sv (/tb_lab1_g8_p3/dut0) - Default
Ln#
1 // X = E'T' + E'U
2 // Y = U' + G'
3 module lab1_g8_p3(
4     input logic g, t, u, e,
5     output logic x,y
6 );
7
8
9     assign x = ~e&~t | ~e&u;
10
11     assign y = ~u | ~g;
12
13 endmodule


```

 


Devre Şemaları:

 

Quartus:

Flow Summary	
 <<Filter>>	
Flow Status	Successful - Fri Apr 28 01:31:38 2023
Quartus Prime Version	22.1std.1 Build 917 02/14/2023 SC Lite Edition
Revision Name	lab1_g8_p3
Top-level Entity Name	lab1_g8_p3
Family	MAX 10
Device	10M08DAF484C8G
Timing Models	Final
Total logic elements	3 / 8,064 (< 1 %)
Total registers	0
Total pins	6 / 250 (2 %)
Total virtual pins	0
Total memory bits	0 / 387,072 (0 %)
Embedded Multiplier 9-bit elements	0 / 48 (0 %)
Total PLLs	0 / 2 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 1 (0 %)

Analysis & Synthesis Summary	
 <<Filter>>	
Analysis & Synthesis Status	Successful - Fri Apr 28 01:31:30 2023
Quartus Prime Version	22.1std.1 Build 917 02/14/2023 SC Lite Edition
Revision Name	lab1_g8_p3
Top-level Entity Name	lab1_g8_p3
Family	MAX 10
Total logic elements	2
Total registers	0
Total pins	6
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

Analysis & Synthesis Resource Usage Summary

<<Filter>>

	Resource	Usage
1	Estimated Total logic elements	2
2		
3	Total combinational functions	2
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	0
2	-- 3 input functions	1
3	-- <=2 input functions	1
5		
6	▼ Logic elements by mode	
1	-- normal mode	2
2	-- arithmetic mode	0
7		
8	▼ Total registers	0
1	-- Dedicated logic registers	0
2	-- I/O registers	0
9		
10	I/O pins	6
11		
12	Embedded Multiplier 9-bit elements	0
13		
14	Maximum fan-out node	u~input
15	Maximum fan-out	2
16	Total fan-out	13
17	Average fan-out	0.93

